

So far we considered only emf and R in the circuits. What if we use capacitors?

Capacitors in circuits

A new way of looking at problems:

Until now: charges at rest or constant currents


When capacitors present: currents vary over time

Consider the following situation:

A capacitor C with charge $Q_0 \rightarrow V_0 = Q_0/C$

A resistor R in series connected by switch s

What happens when switch s is closed?

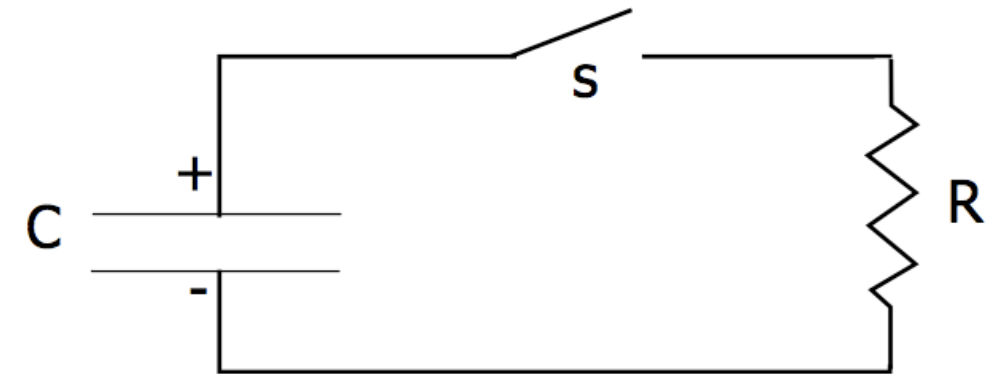

Discharging capacitors: qualitative

Before switch s is closed:

Difference in potential between C plates: V_0


No current circulating in the circuit (open)

After switch s is closed:

Difference in potential between capacitor plates will induce current I

As I flows, charge difference on capacitor decreases

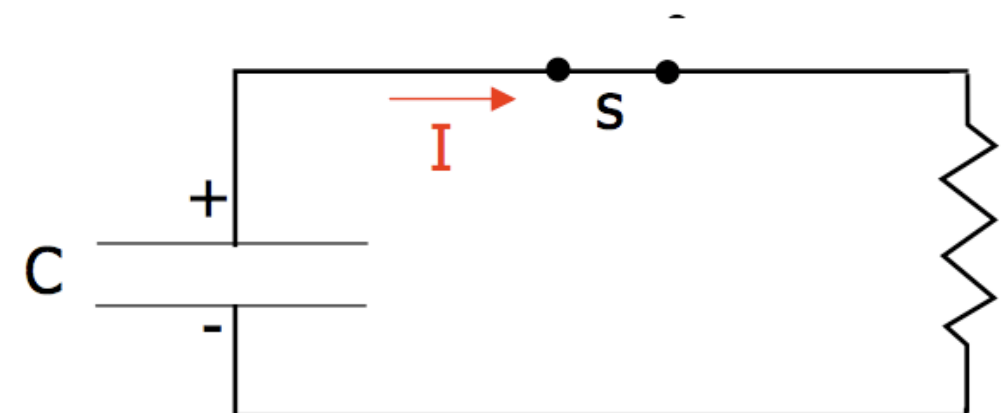$\rightarrow VC$ decreases $\rightarrow I$ decreases over time



Discharging capacitors: quantitative

Apply second Kirchhoff's law:

EMF supplied by capacitor C: $V=Q/C$

Note: this is true at any moment in time $\rightarrow Q(t) \rightarrow V(t)$

Voltage drop across the resistor: $-IR$

$$\frac{Q}{C} - IR = 0$$

Not useful in this form since $I=I(Q)$

$I=-dQ/dt$ (- sign because C is losing charge)

$$\frac{Q}{C} + R \frac{dQ}{dt} = 0$$

Easy integral yields to exponential decay of the charge:

$$\frac{Q}{C} + R \frac{dQ}{dt} = 0 \Rightarrow \frac{dQ}{Q} = -\frac{1}{RC} dt \Rightarrow \int_0^t \frac{dQ}{Q} = -\frac{1}{RC} \int_0^t dt$$

$$\Rightarrow \ln Q(t) - \ln Q(0) = -\frac{t}{RC} \Rightarrow \ln \frac{Q(t)}{Q_0} = -\frac{t}{RC}$$

$$\Rightarrow \frac{Q(t)}{Q_0} = e^{-\frac{t}{RC}} \Rightarrow Q(t) = Q_0 e^{-\frac{t}{RC}} = Q_0 e^{-\frac{t}{\tau}}$$

$\tau = RC$ is called "decay constant" of the circuit

Solution of RC circuit

Solution:
$$Q(t) = Q_0 e^{-\frac{t}{RC}}$$

Exponential decay of charge stored in capacitor

What are the units of RC?

cgs: $[R]=\text{statvolts /esu}$; $[C]=\text{esu/statvolt} \rightarrow [RC]=\text{s}$

SI: $[R]=\text{V/A}$; $[C]=\text{C/V}$; $\text{A}=\text{C/s} \rightarrow [RC]=\text{s}$

$\tau=RC$ is called "decay constant" of the circuit

After a time RC, the charge decreased by $1/e$ wrt original value

Derive the current:

$$I(t) = -\frac{dQ}{dt} = Q_0 \frac{d}{dt} \left(e^{-\frac{t}{RC}} \right) = \frac{Q_0}{RC} e^{-\frac{t}{RC}}$$

Same exponential decay as for $Q(t)$

Charging capacitors

Now 3 elements in circuit: EMF, capacitor and resistor


Capacitor starts uncharged

What happens when switch s is closed?

When s is closed, current will suddenly flow and C will charge

As C charges, E opposite to EMF builds up and slows down current

$I(t)$ stops when V_C reaches V

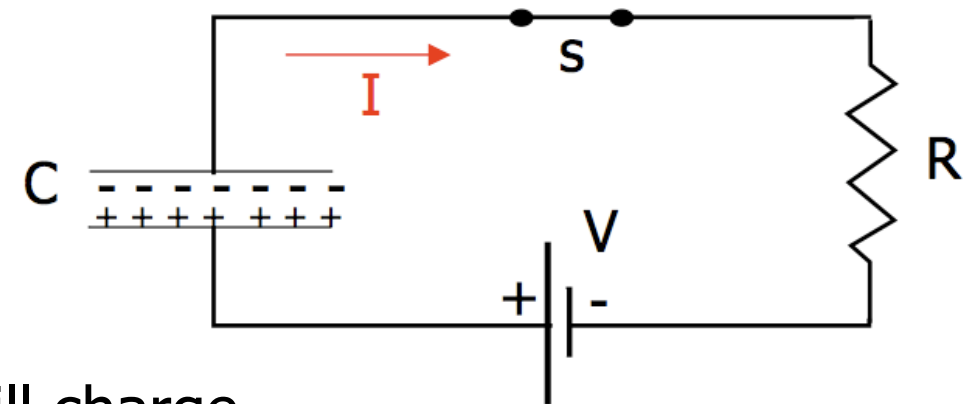

Charging capacitor: solve the circuit $V - \frac{Q}{C} - IR = 0$

Solve using Kirchhoff's second law:

$$I(t) = +dQ/dt$$

+ because the capacitor is now charging!

First order differential equation

$$R \frac{dQ}{dt} + \frac{Q}{C} - V = 0$$

Details of integration


$$R \frac{dQ}{dt} + \frac{Q}{C} - V = 0 \Rightarrow \frac{dQ}{dt} = -\frac{Q - VC}{RC}$$

$$Q' = Q - CV \Rightarrow \frac{dQ'}{dt} = -\frac{Q'}{RC} \Rightarrow \frac{dQ'}{Q'} = -\frac{dt}{RC}$$


Integrating between $t = 0$ and t :

$$\int_{Q=0}^{Q=Q(t)} \frac{dQ'}{Q'} = -\frac{1}{RC} \int_{t=0}^{t=t} dt \Rightarrow \ln \frac{Q'(t)}{Q'(0)} = \ln \frac{Q(t) - CV}{-CV} = -\frac{t}{RC}$$
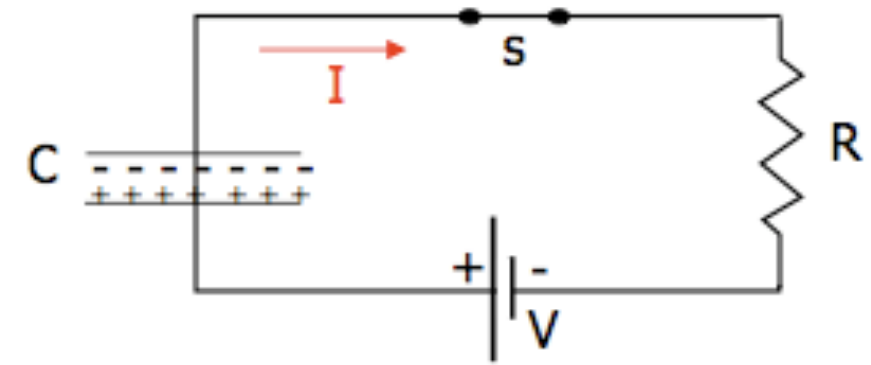
$$\Rightarrow \frac{Q(t) - CV}{-CV} = e^{-\frac{t}{RC}} \Rightarrow Q(t) = CV \left(1 - e^{-\frac{t}{RC}} \right) \quad \text{Solution}$$



Graphical solution

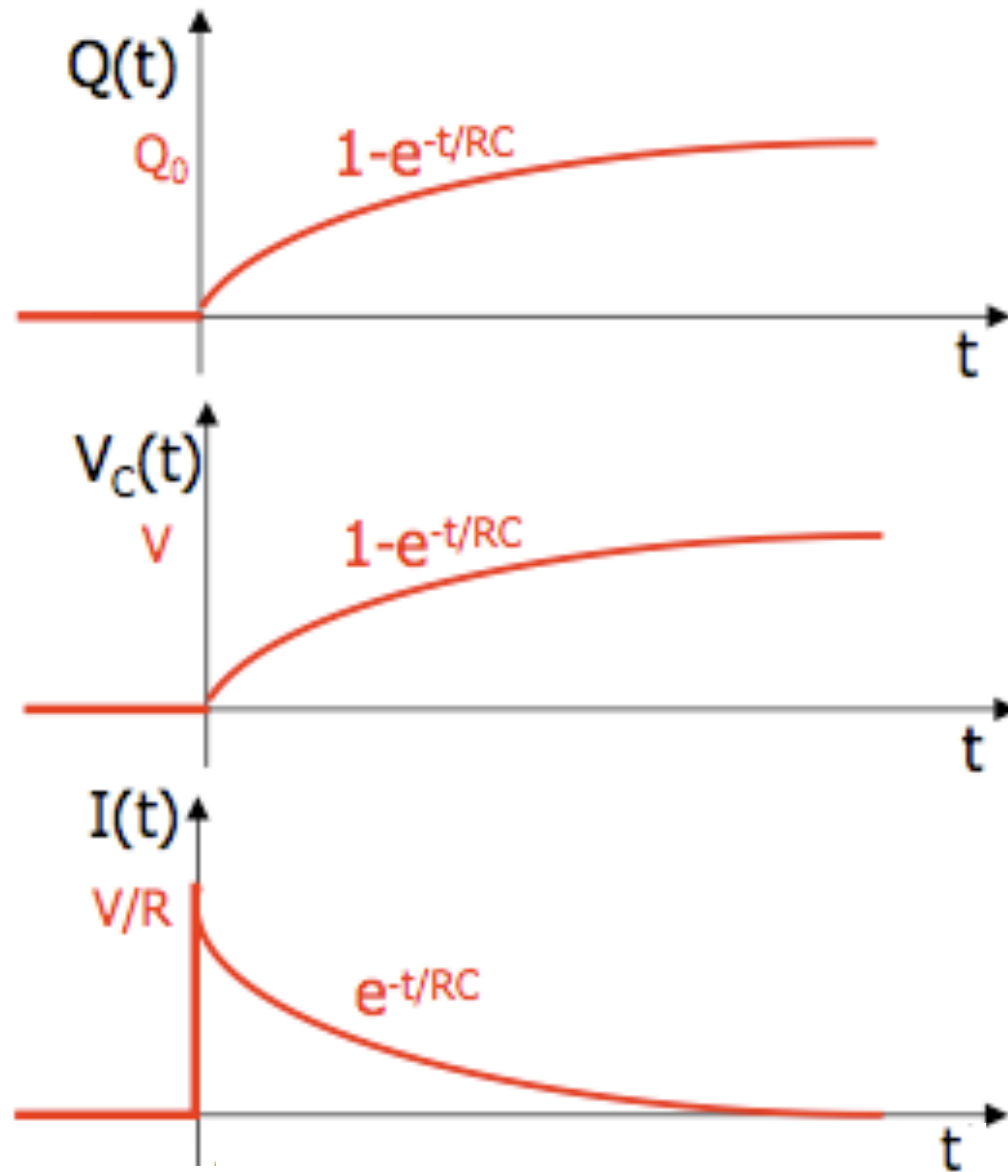

$$Q(t) = CV \left(1 - e^{-\frac{t}{RC}} \right)$$

$$V_C(t) = \frac{Q(t)}{C} = V \left(1 - e^{-\frac{t}{RC}} \right)$$

$$I(t) = \frac{dQ(t)}{dt} = \frac{V}{R} e^{-\frac{t}{RC}}$$

Important comments

Solution of RC circuit:

$$V_C(t) = \frac{Q(t)}{C} = V \left(1 - e^{-\frac{t}{RC}} \right) \quad I(t) = \frac{dQ(t)}{dt} = \frac{V}{R} e^{-\frac{t}{RC}}$$

Are Kirchhoff's laws valid at any moment in time?

$$V - \frac{Q}{C} - IR = V - V \left(1 - e^{-\frac{t}{RC}} \right) - R \frac{V}{R} e^{-\frac{t}{RC}} = 0 \quad \text{OK!}$$

Asymptotic behavior of the capacitor:

At $t = 0$: $I = V/R$ as if C were a short circuit

At $t = \text{infinity}$, $I = 0$ as if C were an open circuit

Conclusion: no need to solve the differential equation!

Solution is an exponential with time constant RC

Asymptotic behavior of C gives initial/final values for $V(t)$ and $I(t)$

Time constant of RC circuit

Simple RC circuit with

$$V_{emf} = 3 \text{ V}$$



$$C = 1.3 \text{ F}$$

$$R = 11.7 \text{ } \Omega$$

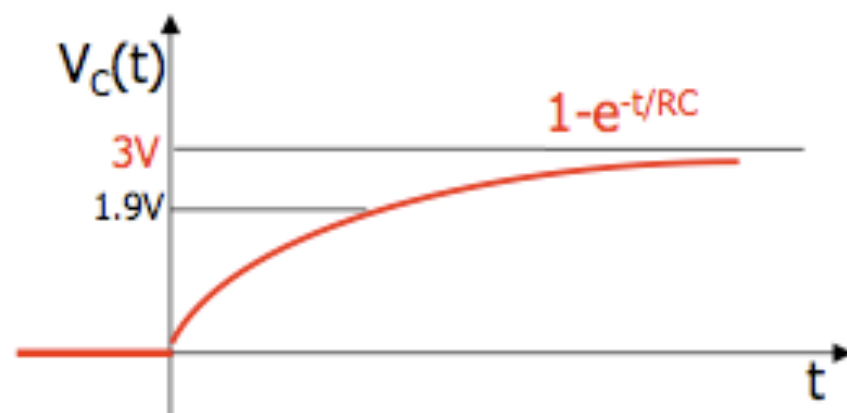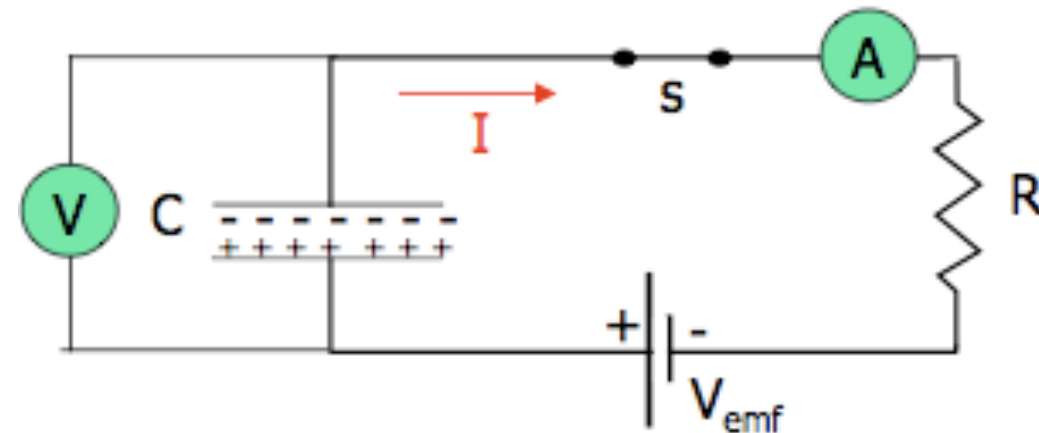Questions:

What are V_C and I ?

Verify that time constant is RC : how long does it take to charge C ?



$$V_C(t) = V_{emf} \left(1 - e^{-\frac{t}{RC}} \right) \quad \text{Note: } R \text{ and } C \text{ VERY large!}$$

$$RC = 15.2 \text{ s}$$

If formula is correct \rightarrow

$$V_C = V (1 - 1/e) = 1.9 \text{ V} \quad \text{when } t = 15.2$$

Verify time constant

RC circuit with

V_{EMF} = squared 5 V pulses




Variable C initially = $0.3 \mu\text{F}$

Variable R_2 initially = 400Ω

$R_1 = 100 \Omega$

Display on scope V_C and $I(R_1)$

Verify $RC = 150 \mu\text{s}$

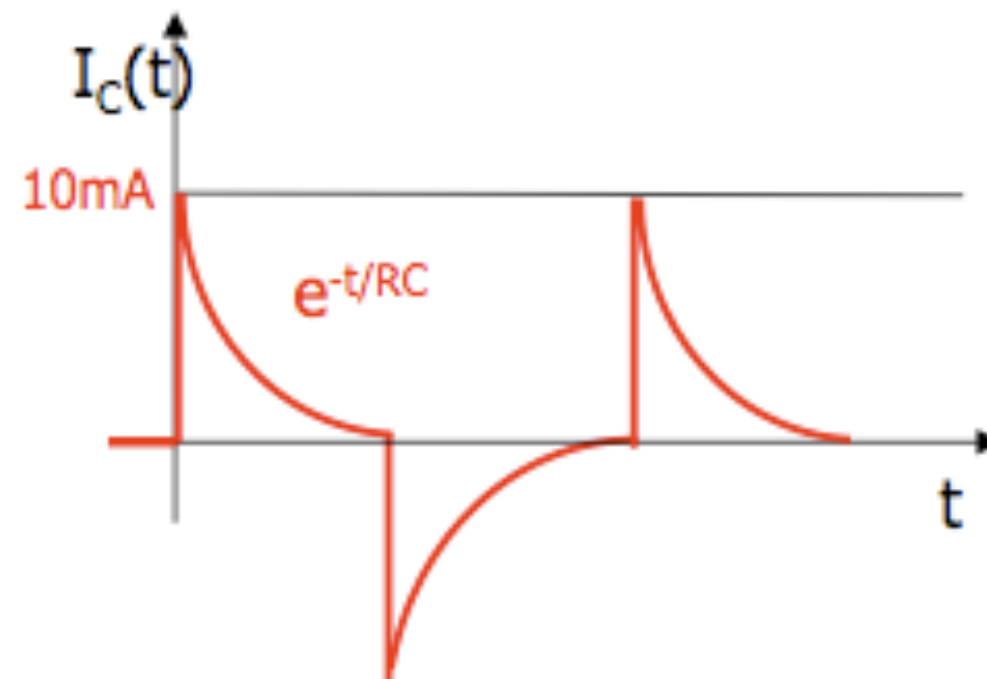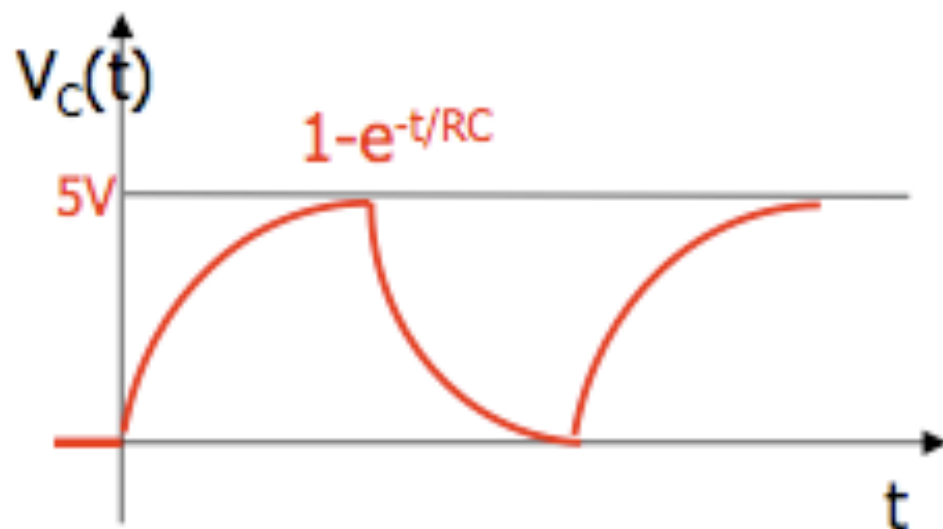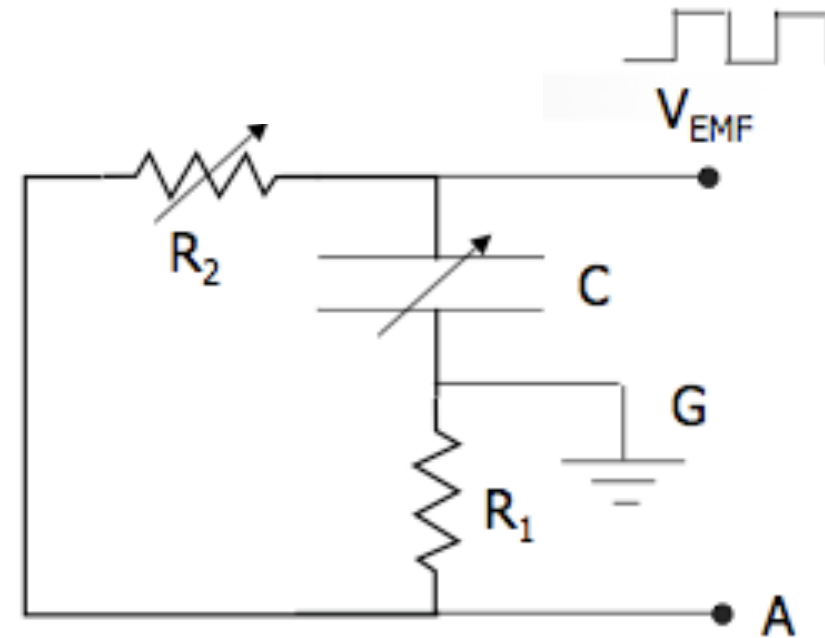

Verify time constant

RC circuit with

V_{EMF} = squared 5 V pulses

Variable C initially = $0.3 \mu\text{F}$

Variable R_2 initially = 400Ω

$R_1 = 100 \Omega$


Let's now change the settings!

What happens when we double C?

$\tau_1 = RC' = 2RC = 2\tau_0 \rightarrow V (I_{AG})$ raises (falls) twice as fast

How should we change R_2 to have the same effect?

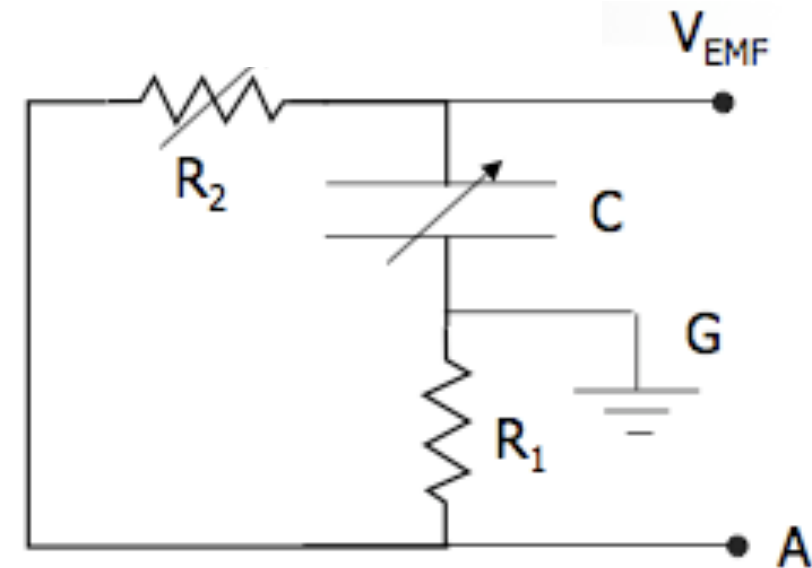
$R' = 2R = 2(R_1 + R_2) \rightarrow R_2': 400 \rightarrow 900 \Omega$



More complicated RC circuits

What if the RC circuit is more than just a series of R and C?

Consider the following circuit:

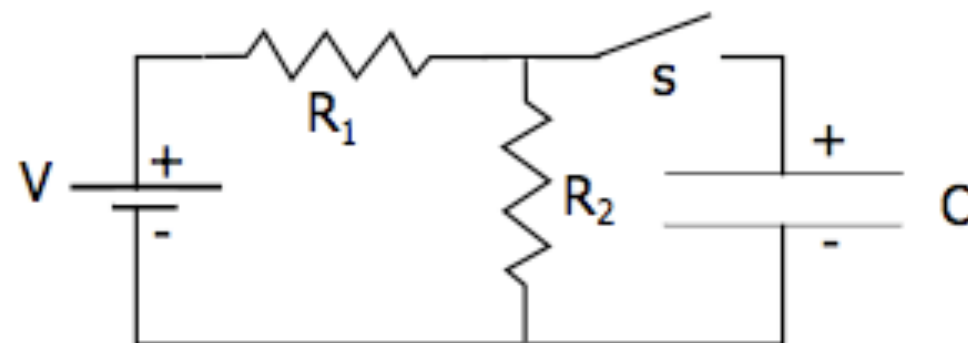

Calculate $Q(t)$ on the capacitor

Solution:

Kirchoff's laws will solve it: TEDIIOUS!

Use Thevenin's Theorem!

Thevenin equivalence


Thevenin's theorem:

Any combination of resistors and EMFs with 2 terminals can be replaced with a series circuit of an emf V_{OC} and a resistor R_T where

V_{OC} is the open circuit voltage

$R_T = V_{OC}/I_{short}$ where I_{short} is the current going through the shorted terminals
or $R_T = R_{eq}$ with all the EMF shorted

In our case:

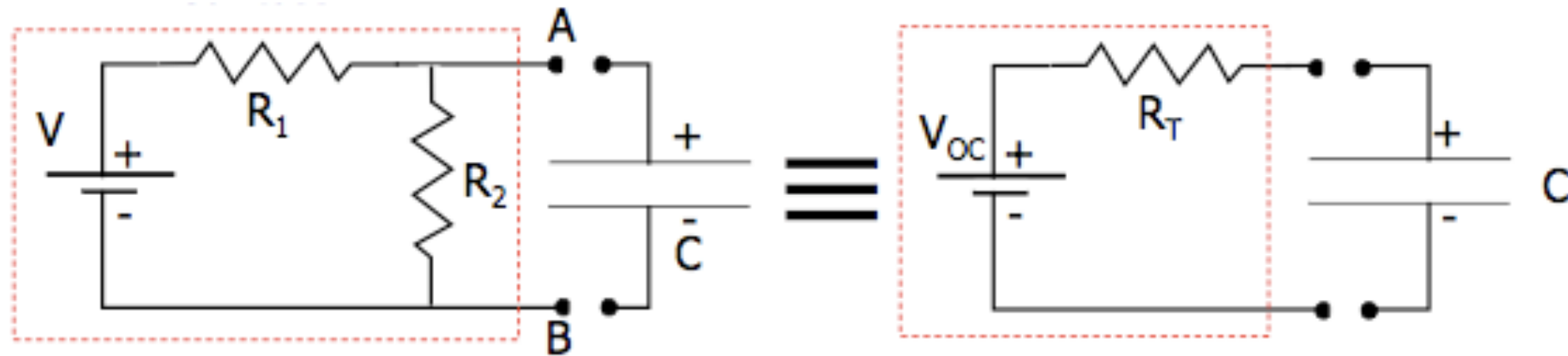

Once the circuit is reduced, the solution is known: $Q(t) = CV_{OC} \left(1 - e^{-\frac{t}{R_T C}} \right)$

Thevenin's demonstration

Prove that V_{OC} is the open circuit voltage

Since

$$Q(t) = CV_{OC} \left(1 - e^{-\frac{t}{R_T C}} \right) \Rightarrow V_C(t) = V_{OC} \left(1 - e^{-\frac{t}{R_T C}} \right)$$

So V_{OC} is the asymptotic V for the capacitor

Since for $t \rightarrow \text{infinity}$, $C \rightarrow \text{open circuit}$: $V_{OC} = V$ of the open circuit

Prove that $R_T = V_{OC}/I_{short}$ with I_{short} = current through shorted terminals


There is only one current going through the reduced circuit

At $t = 0$, C behaves like a short \rightarrow At $t = 0$ $I_{short} = V_{OC}/R_T$

$$\rightarrow R_T = V_{OC}/I_{short}$$

Solve the actual problem

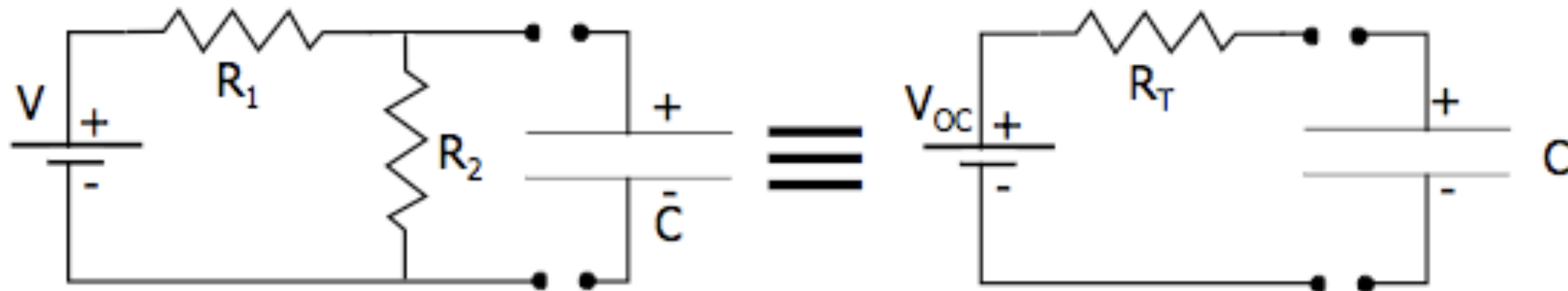Calculate V_{OC} and $R_T = V_{OC}/I_{short}$ for our problem:



$$V_{OC} = \frac{V}{R_1 + R_2} R_2$$

Shorting C is makes R_2 irrelevant in the circuit:

$$I_{short} = \frac{V}{R_1}$$

$$\Rightarrow Q(t) = C \frac{VR_2}{R_1 + R_2} \left(1 - e^{-\frac{t(R_1 + R_2)}{R_1 R_2 C}} \right)$$

$$R_{Thevenin} = \frac{V_{OC}}{I_{short}} = \frac{R_1 R_2}{R_1 + R_2}$$


$$\Rightarrow I(t) = \frac{V}{R_1} e^{-\frac{t(R_1 + R_2)}{R_1 R_2 C}}$$

Note : This is $R_1 \parallel R_2$, same resistance we would get if we shorted EMF!

Thoughts on Thevenin

The importance of Thevenin:

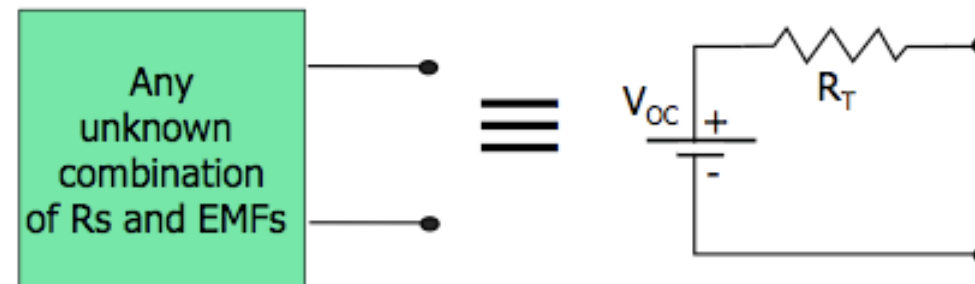When we have a messy system or resistors and EMFs, we can reduce it to a simple R+EMF in series just measuring I_{short} and V_{open} :



Careful:

Thevenin works only when the elements in the box follow Ohm's law, i.e. linear relation between V and I

Oscillating circuit

RC circuit with:

$$V_{\text{EMF}} = 1 \text{ kV}$$

$$C = 0.1 \mu\text{F}$$

$$R = 2.5 \text{ M}\Omega$$

Fluorescent light in parallel with capacitor

($R_{\text{FL}} \ll R$ when current flows; \sim infinite otherwise)

Why is light flashing at $f \sim 1\text{Hz}$?


Initially the capacitor will start charging (no current thru lamp)

When $V_C >$ certain value $\sim 1\text{kV}$ current flows thru fluorescent light

discharging the capacitor very quickly

The process will start again

$$f \sim 1/\tau = 1/RC = 4 \text{ Hz}$$

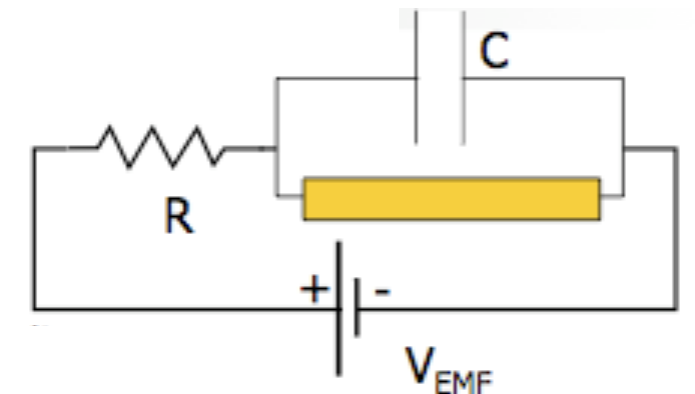

Note: charging and discharging time constants are very different!

Charging: fluorescent light is \sim open circuit: $\tau_{\text{charge}} = RC$

Discharge: fluorescent light has a (very small) resistance R_{FL}

Thevenin: $R_T = R \parallel R_{\text{FL}} \sim R_{\text{FL}}$


$\tau_{\text{discharge}} = R_T C \sim R_{\text{FL}} C \ll \tau_{\text{charge}}$

Norton's theorem

Any combination of resistors and EMFs with 2 terminals can be replaced with a parallel combination of a current generator I_N and a resistor R_T where

R_T is the equivalent resistance of the circuit with all the EMF shorted and all the current sources open (same as Thevenin!)

$I_N = V_{\text{OC}}/R_T$

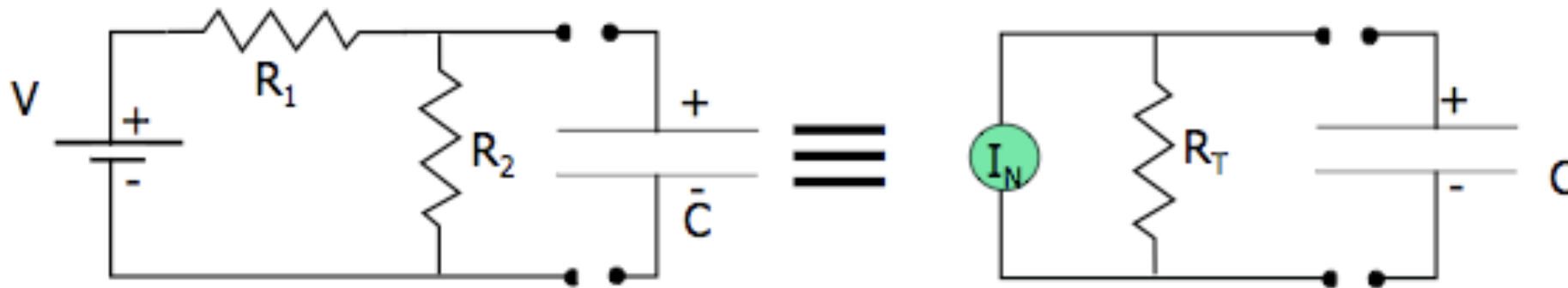

$$R_T = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_N = \frac{V_{\text{OC}}}{R_T} = \frac{V R_2}{R_1 + R_2} \frac{R_1 + R_2}{R_1 R_2} = \frac{V}{R_1}$$